

Lab 9-10 – Nano-processor Design Competition

CS1050 Computer Organization and Digital Design

Dept. of Computer Science and Engineering, University of Moratuwa

Presented By – S.A.C.H.Gunapala
210190R


G.V.H.H.B.Jayarathna
210242F

Assigned Lab Task.

This lab in particular is a team project. Teams of two are assigned to design and test a 4-bit processor on Basys3 FPGA which is capable of executing 4 instructions using a Programmable ROM.

Assembly program and its machine code representation.

Given a 12-bit instruction as follows,

 

Let's see some examples of machine code representation of some assembly language code,

Machine Code	Assembly Language
100010000011	MOV R1, 3
101110000001	MOV R7, 1
001110010000	ADD R7, R1
011110000000	NEG R7
110010000110	JZR R1, 6

Possible commands and other useful commands,

Command	Assembly Language Command
00	ADD (adds the data in two registers)
10	MOVI (moves data to a register)
01	NEG (gets the two's compliment)
11	JZR (jump command if the given register has 0000 to an instruction)

Register Selection,

Command	Selected Register
000	R0
001	R1
010	R2
011	R3
100	R4
101	R5
110	R6
111	R7

Last 4 digits display the immediate data input to the nanoprocessor.

VHDL Codes.

- **Instructions Decoder.**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity InstructionDecoder is
    Port ( I : in STD_LOGIC_VECTOR (11 downto 0);
          Reg_Check : in STD_LOGIC_VECTOR (3 downto 0);
          Reg_EN : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Sel0 : out STD_LOGIC_VECTOR (2 downto 0);
```

```

    Reg_Sel1 : out STD_LOGIC_VECTOR (2 downto 0);

    Address : out STD_LOGIC_VECTOR (2 downto 0);

    d_value : out STD_LOGIC_VECTOR (3 downto 0);

    Jump : out STD_LOGIC;

    Load_Sel : out STD_LOGIC;

    Add_Sub : out STD_LOGIC);

end InstructionDecoder;

```

architecture Behavioral of InstructionDecoder is

```

signal Jump_Temp : std_logic;

```

```

begin

```

```

    d_value <= I(3 downto 0);

    Reg_EN <= I(9 downto 7);

    Reg_Sel1 <= I(9 downto 7);

    Reg_Sel0 <= I(6 downto 4);

    Add_Sub <= (not I(11)) and I(10);

    Jump_Temp <= I(11) and I(10);

    Load_Sel <= I(11) and (not I(10));

    Address <= I(2 downto 0);

    Jump <= Jump_Temp and (not (Reg_Check(0) or Reg_Check(1) or Reg_Check(2) or Reg_Check(3)));

```

```

end Behavioral;

```

- **Mux 2way 4-bit.**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity Mux_2way_4bit is
```

```
    Port ( S : in STD_LOGIC;
```

```
          D0 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D1 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          Y : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end Mux_2way_4bit;
```

```
architecture Behavioral of Mux_2way_4bit is
```

```
    signal S_vec :std_logic_vector(3 downto 0);
```

```
begin
```

```
    S_vec <= (others => S); -- Assigning S to every element of S_vec
```

```
    Y <= (D0 and not S_vec) or (D1 and S_vec);
```

```
end Behavioral;
```

- **LUT for 7-Segment Display.**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity LUT_16_7 is
  Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
        data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is

  type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

  signal sevenSegment_ROM : rom_type := (
    "1000000", --0
    "1111001", --1
    "0100100", --2
    "0110000", --3
    "0011001", --4
    "0010010", --5
    "0000010", --6
    "1111000", --7
    "0000000", --8
    "0010000", --9
    "0001000", --a
    "0000011", --b
    "1000110", --c
    "0100001", --d
    "0000110", --e
    "0001110" --f
  );

begin

  data <= sevenSegment_ROM(to_integer(unsigned(address)));

end Behavioral;
```

- **Programmable ROM.**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity PROM is
```

```
    Port ( Mem_Sel : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          I : out STD_LOGIC_VECTOR (11 downto 0));
```

```
end PROM;
```

```
architecture Behavioral of PROM is
```

```
    type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);
```

```
    signal instruction_ROM : rom_type := (
```

```
        --CHANGE INSTRUCTIONS HERE
```

```
        "101110000000", --MOV R7, 0
```

```
        "100010000001", --MOV R1, 1
```

```
        "100100000010", --MOV R2, 2
```

```
        "100110000011", --MOV R3, 3
```

```
        "001110010000", --ADD R7, R1
```

```
        "001110100000", --ADD R7, R2
```

```
        "001110110000", --ADD R7, R3
```

```
"110000000111" --JZR R0, 7  
);
```

```
begin
```

```
I <= instruction_ROM(to_integer(unsigned(Mem_Sel)));
```

```
end Behavioral;
```

- **Program Counter.**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity PC is
```

```
Port ( Jump : in STD_LOGIC;
```

```
Address : in STD_LOGIC_VECTOR (2 downto 0);
```

```
Clk : in STD_LOGIC;
```

```
Res : in STD_LOGIC;
```

```
M : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end PC;
```

```
architecture Behavioral of PC is
```

```

component RCA_3
  Port ( A : in STD_LOGIC_VECTOR (2 DOWNTO 0);
        S : out STD_LOGIC_VECTOR (2 DOWNTO 0);
        C_out : out STD_LOGIC);
end component;

```

```

component Mux_2way_3bit
  Port ( S : in STD_LOGIC;
        D0 : in STD_LOGIC_VECTOR (2 downto 0);
        D1 : in STD_LOGIC_VECTOR (2 downto 0);
        Y : out STD_LOGIC_VECTOR (2 downto 0));
end component;

```

```

component PCReg
  Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
        Res : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (2 downto 0));
end component;

```

```

SIGNAL PC_out, adder_out, Mux_out : STD_LOGIC_VECTOR(2 downto 0);
SIGNAL C_out_adder: STD_LOGIC;

```

```

begin
  adder_3_bit: RCA_3
  port map(
    A => PC_out,
    S => adder_out,
    C_out => C_out_adder);

```



```
Mux_2way_3bit_0: Mux_2way_3bit
```

```
port map(
```

```
    S => Jump,
```

```
    D0 => adder_out,
```

```
    D1 => Address,
```

```
    Y => Mux_out);
```

```
ProgramCounter: PCReg
```

```
port map(
```

```
    D => Mux_out,
```

```
    Res => Res,
```

```
    Clk => Clk,
```

```
    Q => PC_out);
```

```
M <= PC_out;
```

```
end Behavioral;
```

- **Program Counter Register(PC_reg).**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

entity PCReg is

Port (D : in STD_LOGIC_VECTOR (2 downto 0);

Res : in STD_LOGIC;

Clk : in STD_LOGIC;

Q : out STD_LOGIC_VECTOR (2 downto 0));

end PCReg;

architecture Behavioral of PCReg is

component D_FF

port (

D : in STD_LOGIC;

Res: in STD_LOGIC;

Clk : in STD_LOGIC;

Q : out STD_LOGIC);

end component;

begin

D_FF0 : D_FF

port map (

D => D(0),

Res => Res,

Clk => Clk,

Q => Q(0));

D_FF1 : D_FF

port map (

D => D(1),

```
Res => Res,  
Clk => Clk,  
Q => Q(1));
```

```
D_FF2 : D_FF
```

```
port map (
```

```
    D => D(2),
```

```
    Res => Res,
```

```
    Clk => Clk,
```

```
    Q => Q(2));
```

```
end Behavioral;
```

- **D_FF**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity D_FF is
```

```
    Port ( D : in STD_LOGIC;
```

```
          Res : in STD_LOGIC;
```

```
          Clk : in STD_LOGIC;
```

```
          Q : out STD_LOGIC);
```

```
end D_FF;
```

```
architecture Behavioral of D_FF is
```

```
    signal Q_reg : std_logic := '0';
```

```
begin
```

```
    process (Clk) begin
```

```
        if (rising_edge(Clk)) then
```

```
            if Res = '1' then
```

```
                Q_reg <= '0';
```

```

        else
            Q_reg <= D;
        end if;
    end if;
    Q <= Q_reg;
end process;
end Behavioral;

```

- **Mux_2way_3bit**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity Mux_2way_3bit is
    Port ( S : in STD_LOGIC;
          D0 : in STD_LOGIC_VECTOR (2 downto 0);
          D1 : in STD_LOGIC_VECTOR (2 downto 0);
          Y : out STD_LOGIC_VECTOR (2 downto 0));
end Mux_2way_3bit;

```

```

architecture Behavioral of Mux_2way_3bit is

```

```

    signal S_vec :std_logic_vector(2 downto 0);

```

```

begin

```

```

    S_vec <= (others => S); -- Assigning S to every element of S_vec
    Y <= (D0 and not S_vec) or (D1 and S_vec);

```

```

end Behavioral;

```

- **Adder_3_bit**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating

```

```

-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity RCA_3 is
  Port ( A : in STD_LOGIC_VECTOR (2 DOWNTO 0);
        S : out STD_LOGIC_VECTOR (2 DOWNTO 0);
        C_out : out STD_LOGIC);
end RCA_3;

architecture Behavioral of RCA_3 is
  component FA
    port (
      A: in STD_LOGIC;
      B: in STD_LOGIC;
      C_in: in STD_LOGIC;
      S: out STD_LOGIC;
      C_out: out STD_LOGIC);
  end component;

  SIGNAL FA0_C,FA1_C : STD_LOGIC;

begin

  FA_0 : FA
    port map(
      A => A(0),
      B => '1',
      C_in => '0',
      S => S(0),
      C_out => FA0_C);

  FA_1 : FA
    port map(
      A => A(1),
      B => '0',
      C_in => FA0_C,
      S => S(1),
      C_out => FA1_C);

  FA_2 : FA
    port map(
      A => A(2),
      B => '0',
      C_in => FA1_C,
      S => S(2),
      C_out => C_out);

end Behavioral;

```

- **Add/Sub Unit.**

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

entity Add_Sub_unit is

```
    Port ( D : in STD_LOGIC_VECTOR (31 downto 0);
          RegSel0 : in STD_LOGIC_VECTOR (2 downto 0);
          RegSel1 : in STD_LOGIC_VECTOR (2 downto 0);
          AddSub : in STD_LOGIC; -- 0 is adder, 1 is subtracter
          Overflow : out STD_LOGIC;
          Zero : out STD_LOGIC;
          Output : out STD_LOGIC_VECTOR (31 downto 0);
          RegCheck : out STD_LOGIC_VECTOR (31 downto 0));
```

end Add_Sub_unit;

architecture Behavioral of Add_Sub_unit is

component RCAS_4

```
    Port ( A : in STD_LOGIC_VECTOR(31 downto 0);
          B : in STD_LOGIC_VECTOR(31 downto 0);
          Func : in STD_LOGIC; -- 0 is adder, 1 is subtracter
```

```
        S : out STD_LOGIC_VECTOR(3 downto 0);  
        C_out : out STD_LOGIC);  
end component;
```

```
component Mux_8way_4bit  
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);  
          D : in STD_LOGIC_VECTOR (31 downto 0);  
          Y : out STD_LOGIC_VECTOR (3 downto 0));  
end component;
```

```
SIGNAL Mux0_out, Mux1_out, result: STD_LOGIC_VECTOR(3 downto 0);
```

```
SIGNAL Overflow_flag: STD_LOGIC;
```

```
begin
```

```
    Mux_8way_4bit_0 : Mux_8way_4bit  
    port map(  
        S => RegSel0,  
        D => D,  
        Y => Mux0_out);
```

```
    Mux_8way_4bit_1 : Mux_8way_4bit  
    port map(  
        S => RegSel1,  
        D => D,  
        Y => Mux1_out);
```

```
    RCAS_0 : RCAS_4  
    port map(  
        A => Mux0_out,  
        B => Mux1_out,
```

```

Func => AddSub,

S => result,

C_out => Overflow_flag);

Overflow <= Overflow_flag;

Output <= result;

RegCheck <= Mux0_out;

Zero <= NOT( result(0) OR result(1) OR result(2) OR result(3) OR Overflow_flag);

```

```

end Behavioral;

```

- **Mux_8way_4bit.**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity Mux_8way_4bit is
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
          D : in STD_LOGIC_VECTOR (31 downto 0);
          Y : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_8way_4bit;

```

```

architecture Behavioral of Mux_8way_4bit is

```

```

    component Decoder_3_to_8
    port (
        address: in std_logic_vector(2 downto 0);
        data: out std_logic_vector(7 downto 0));
    end component;

```

```

    signal decoded_S :std_logic_vector(7 downto 0);
    signal S0_vec :std_logic_vector(3 downto 0);
    signal S1_vec :std_logic_vector(3 downto 0);
    signal S2_vec :std_logic_vector(3 downto 0);
    signal S3_vec :std_logic_vector(3 downto 0);

```



```

signal S4_vec :std_logic_vector(3 downto 0);
signal S5_vec :std_logic_vector(3 downto 0);
signal S6_vec :std_logic_vector(3 downto 0);
signal S7_vec :std_logic_vector(3 downto 0);

```

```

begin

```

```

    LUT_Decoder : Decoder_3_to_8
    port map(
        address => S,
        data => decoded_S);

```

```

    S0_vec <= (others => decoded_S(0)); -- Assigning decoded_s(0) to every element of S0_vec
    S1_vec <= (others => decoded_S(1));
    S2_vec <= (others => decoded_S(2));
    S3_vec <= (others => decoded_S(3));
    S4_vec <= (others => decoded_S(4));
    S5_vec <= (others => decoded_S(5));
    S6_vec <= (others => decoded_S(6));
    S7_vec <= (others => decoded_S(7));

```

```

    Y <= (D(3 downto 0) and S0_vec) or (D(7 downto 4) and S1_vec) or (D(11 downto 8) and S2_vec) or
    (D(15 downto 12) and S3_vec) or (D(19 downto 16) and S4_vec) or (D(23 downto 20) and S5_vec) or (D(27
    downto 24) and S6_vec) or (D(31 downto 28) and S7_vec);

```

```

end Behavioral;

```

- **RCAS (Ripple carry Adder/Subtractor).**

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity RCAS_4 is

```

```

    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          Func : in STD_LOGIC; -- 0 is adder, 1 is subtracter
          S : out STD_LOGIC_VECTOR(3 downto 0);
          C_out : out STD_LOGIC);

```

```

end RCAS_4;

```

architecture Behavioral of RCAS_4 is

component FA

port (

A: in STD_LOGIC;

B: in STD_LOGIC;

C_in: in STD_LOGIC;

S: out STD_LOGIC;

C_out: out STD_LOGIC);

end component;

SIGNAL FA0_C,FA1_C,FA2_C,FA3_C : STD_LOGIC;

SIGNAL BS : STD_LOGIC_VECTOR(3 downto 0);

begin

FA_0 : FA

port map(

A => A(0),

B => BS(0),

C_in => Func,

S => S(0),

C_out => FA0_C);

FA_1 : FA

port map(

A => A(1),

B => BS(1),

C_in => FA0_C,

S => S(1),

C_out => FA1_C);

FA_2 : FA

port map(

A => A(2),

B => BS(2),

C_in => FA1_C,

S => S(2),

C_out => FA2_C);

FA_3 : FA

port map(

A => A(3),

B => BS(3),

C_in => FA2_C,

S => S(3),

C_out => C_out);

BS(0) <= B(0) xor Func;

BS(1) <= B(1) xor Func;

```
BS(2) <= B(2) xor Func;  
BS(3) <= B(3) xor Func;
```

```
end Behavioral;
```

- **FA (Full Adder).**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity FA is  
  Port ( A : in STD_LOGIC;  
        B : in STD_LOGIC;  
        C_in : in STD_LOGIC;  
        S : out STD_LOGIC;  
        C_out : out STD_LOGIC);  
end FA;
```

```
architecture Behavioral of FA is
```

```
component HA  
  port (  
    A : in STD_LOGIC;  
    B : in STD_LOGIC;  
    S : out STD_LOGIC;  
    C : out STD_LOGIC);  
end component;
```

```
SIGNAL HA0_S, HA0_C, HA1_S, HA1_C : STD_LOGIC;
```

```
begin  
HA_0 : HA  
  port map(  
    A => A,  
    B => B,  
    S => HA0_S,  
    C => HA0_C);
```

```
HA_1 : HA  
  port map(  
    A => A,  
    B => B,  
    S => HA1_S,  
    C => HA1_C);
```

```

    A => HA0_S,
    B => C_in,
    S => HA1_S,
    C => HA1_C);

S <= HA1_S;
C_out <= HA0_C OR HA1_C;

end Behavioral;

```

- **HA (Half Adder).**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity HA is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          S : out STD_LOGIC;
          C : out STD_LOGIC);
end HA;

architecture Behavioral of HA is

begin

    S <= A XOR B;
    C <= A AND B;

end Behavioral;

```

- **Reg Bank.**

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values

```

```

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity RegisterBank is
    Port ( R_EN : in STD_LOGIC_VECTOR (2 downto 0);
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Input : in STD_LOGIC_VECTOR (3 downto 0);
          D : out STD_LOGIC_VECTOR (31 downto 0));
end RegisterBank;

architecture Behavioral of RegisterBank is

    component Reg
        Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
              En : in STD_LOGIC;
              Res : in STD_LOGIC;
              Clk : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    component Decoder_3_to_8
        Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
              data : out STD_LOGIC_VECTOR (7 downto 0));
    end component;

    signal EN_vec : std_logic_vector(7 downto 0);

```

```
begin
```

```
LUT_Decoder : Decoder_3_to_8
```

```
PORT MAP(
```

```
    address => R_EN,
```

```
    data => EN_vec
```

```
);
```

```
Reg_0 : Reg
```

```
PORT MAP(
```

```
    D => "0000",
```

```
    En => '1' ,
```

```
    Res => '0',
```

```
    Clk => Clk,
```

```
    Q => D(3 downto 0)
```

```
);
```

```
Reg_1 : Reg
```

```
PORT MAP(
```

```
    D => Input,
```

```
    En => EN_vec(1) ,
```

```
    Res => Res,
```

```
    Clk => Clk,
```

```
    Q => D(7 downto 4)
```

```
);
```

```
Reg_2 : Reg
```

```
PORT MAP(
```

```
    D => Input,
```

```
    En => EN_vec(2) ,
```

```
    Res => Res,  
    Clk => Clk,  
    Q => D(11 downto 8)  
);
```

Reg_3 : Reg

```
PORT MAP(  
    D => Input,  
    En => EN_vec(3) ,  
    Res => Res,  
    Clk => Clk,  
    Q => D(15 downto 12)  
);
```

Reg_4 : Reg

```
PORT MAP(  
    D => Input,  
    En => EN_vec(4) ,  
    Res => Res,  
    Clk => Clk,  
    Q => D(19 downto 16)  
);
```

Reg_5 : Reg

```
PORT MAP(  
    D => Input,  
    En => EN_vec(5) ,  
    Res => Res,  
    Clk => Clk,  
    Q => D(23 downto 20)  
);
```

```

Reg_6 : Reg
PORT MAP(
    D => Input,
    En => EN_vec(6) ,
    Res => Res,
    Clk => Clk,
    Q => D(27 downto 24)
);

```

```

Reg_7 : Reg
PORT MAP(
    D => Input,
    En => EN_vec(7) ,
    Res => Res,
    Clk => Clk,
    Q => D(31 downto 28)
);

```

```

end Behavioral;

```

- **Decoder_3_to_8(LUT).**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating

```



```

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity Decoder_3_to_8 is
    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
          data : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is

    type rom_type is array (0 to 7) of std_logic_vector(7 downto 0);

    signal decoder_ROM : rom_type := (

        "00000001", --0
        "00000010", --1
        "00000100", --2
        "00001000", --3
        "00010000", --4
        "00100000", --5
        "01000000", --6
        "10000000" --7
    );

begin

    data <= decoder_ROM(to_integer(unsigned(address)));

end Behavioral;

```

- **Register.**

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg;


architecture Behavioral of Reg is


begin
    process (Clk,Res)
    begin
        if (rising_edge(Clk)) then -- respond when clock rises
            if En = '1' then -- Enable should be set
                Q <= D;
            end if;
            if (Res = '1') then
                Q <= "0000";
            end if;
        end if;
    end process;
end Behavioral;

```

```
end if;
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

- **Slow Clock.**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity Slow_Clk is
```

```
    Port ( Clk_in : in STD_LOGIC;
```

```
           Clk_out : out STD_LOGIC);
```

```
end Slow_Clk;
```

```
architecture Behavioral of Slow_Clk is
```

```
    signal count: integer := 1;
```

```
    signal clk_status: std_logic := '0';
```

```
begin
```

```

process(Clk_in) begin
  if (rising_edge(Clk_in)) then
    count <= count + 1;
    --if (count = 5) then
    if(count = 50000000) then
      clk_status <= not clk_status;
      Clk_out <= clk_status;
      count <= 1;
    end if;
  end if;
end process;

end Behavioral;

```

- **NanoProcessor.**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity NanoProcessor is
  Port ( Clk : in STD_LOGIC;
        Seg7input : out std_logic_vector (3 downto 0);

```

```

Reset : in STD_LOGIC;

OverFlow : out STD_LOGIC;

Zero : out STD_LOGIC;

Seg7output : out STD_LOGIC_VECTOR (6 downto 0);

Anode : out std_logic_vector (3 downto 0));

end NanoProcessor;

```

architecture Behavioral of NanoProcessor is

component Slow_Clk

```

Port ( Clk_in : in STD_LOGIC;

       Clk_out : out STD_LOGIC);

end component;

```

component LUT_16_7

```

Port ( result : in STD_LOGIC_VECTOR (3 downto 0);

       data : out STD_LOGIC_VECTOR (6 downto 0));

end component;

```

component RegisterBank

```

Port ( R_EN : in STD_LOGIC_VECTOR (2 downto 0);

       Res : in STD_LOGIC;

       Clk : in STD_LOGIC;

       Input : in STD_LOGIC_VECTOR (3 downto 0);

       D : out STD_LOGIC_VECTOR (31 downto 0));

end component;

```

component Add_Sub_unit

```

Port ( D : in STD_LOGIC_VECTOR (31 downto 0);

       RegSel0 : in STD_LOGIC_VECTOR (2 downto 0);

       RegSel1 : in STD_LOGIC_VECTOR (2 downto 0);

```

```

    AddSub : in STD_LOGIC; -- 0 is adder, 1 is subtracter

    Overflow : out STD_LOGIC;

    Zero : out STD_LOGIC;

    Output : out STD_LOGIC_VECTOR (3 downto 0);

    RegCheck : out STD_LOGIC_VECTOR (3 downto 0));

end component;

```

```

component PC

```

```

    Port ( Jump : in STD_LOGIC;

          Address : in STD_LOGIC_VECTOR (2 downto 0);

          Clk : in STD_LOGIC;

          Res : in STD_LOGIC;

          M : out STD_LOGIC_VECTOR (2 downto 0));

end component;

```

```

component PROM

```

```

    Port ( Mem_Sel : in STD_LOGIC_VECTOR (2 downto 0);

          I : out STD_LOGIC_VECTOR (11 downto 0));

end component;

```

```

component Mux_2way_4bit

```

```

    Port ( S : in STD_LOGIC;

          D0 : in STD_LOGIC_VECTOR (3 downto 0);

          D1 : in STD_LOGIC_VECTOR (3 downto 0);

          Y : out STD_LOGIC_VECTOR (3 downto 0));

end component;

```

```

component InstructionDecoder

```

```

    Port ( I : in STD_LOGIC_VECTOR (11 downto 0);

          Reg_Check : in STD_LOGIC_VECTOR (3 downto 0);

          Reg_EN : out STD_LOGIC_VECTOR (2 downto 0);

```

```

    Reg_Sel0 : out STD_LOGIC_VECTOR (2 downto 0);

    Reg_Sel1 : out STD_LOGIC_VECTOR (2 downto 0);

    Address : out STD_LOGIC_VECTOR (2 downto 0);

    d_value : out STD_LOGIC_VECTOR (3 downto 0);

    Jump : out STD_LOGIC;

    Load_Sel : out STD_LOGIC;

    Add_Sub : out STD_LOGIC);

end component;


signal slow_clk_sig, AddSub,Jump, Load_sel : std_logic;

signal Reg_En,RegSel0, RegSel1, JumpAddress,M : std_logic_vector(2 downto 0);

signal Regbank_input, AddSub_out, RegCheck, d_value : std_logic_vector(3 downto 0);

signal I : std_logic_vector(11 downto 0);

signal D : std_logic_vector(31 downto 0);


begin

    Slow_Clk_0: Slow_Clk

    port map(

        Clk_in => Clk,

        Clk_out => slow_clk_sig

    );


    Reg_bank: RegisterBank

    port map(

        R_EN => Reg_En,

        Res => Reset,

        Clk => slow_clk_sig,

        Input => Regbank_input,

        D => D

    );

```

AddSubUnit: Add_Sub_unit

```
port map(  
    D => D,  
    RegSel0 => RegSel0,  
    RegSel1 => RegSel1,  
    AddSub => AddSub,  
    OverFlow => overflow,  
    Zero => Zero,  
    Output => AddSub_out,  
    RegCheck => RegCheck  
);
```

ProgrammeCounter: PC

```
port map(  
    Jump => Jump,  
    Address => JumpAddress,  
    Clk => slow_clk_sig,  
    Res => Reset,  
    M => M  
);
```

ProgramROM : PROM

```
port map(  
    Mem_Sel => M,  
    I => I  
);
```

LUT_16_7_0: LUT_16_7

```
port map(  
    result => D(31 downto 28),  
    data => Seg7output
```



```
);
```

```
Mux: Mux_2way_4bit
```

```
port map(
```

```
    S => Load_sel,
```

```
    D0 => AddSub_out,
```

```
    D1 => d_value,
```

```
    Y => Regbank_input
```

```
);
```

```
Instruction_decoder: InstructionDecoder
```

```
port map(
```

```
    I => I,
```

```
    Reg_Check => RegCheck,
```

```
    Reg_EN => Reg_En,
```

```
    Reg_sel0 => RegSel0,
```

```
    Reg_sel1 => RegSel1,
```

```
    Address => JumpAddress,
```

```
    d_value => d_value,
```

```
    Jump => Jump,
```

```
    Load_Sel => Load_sel,
```

```
    Add_Sub => AddSub
```

```
);
```

```
Anode <= "1110";
```


```
Seg7input <= D(31 downto 28);
```

Timing Diagrams.


- Nano-Processor.




- Instructions Decoder.

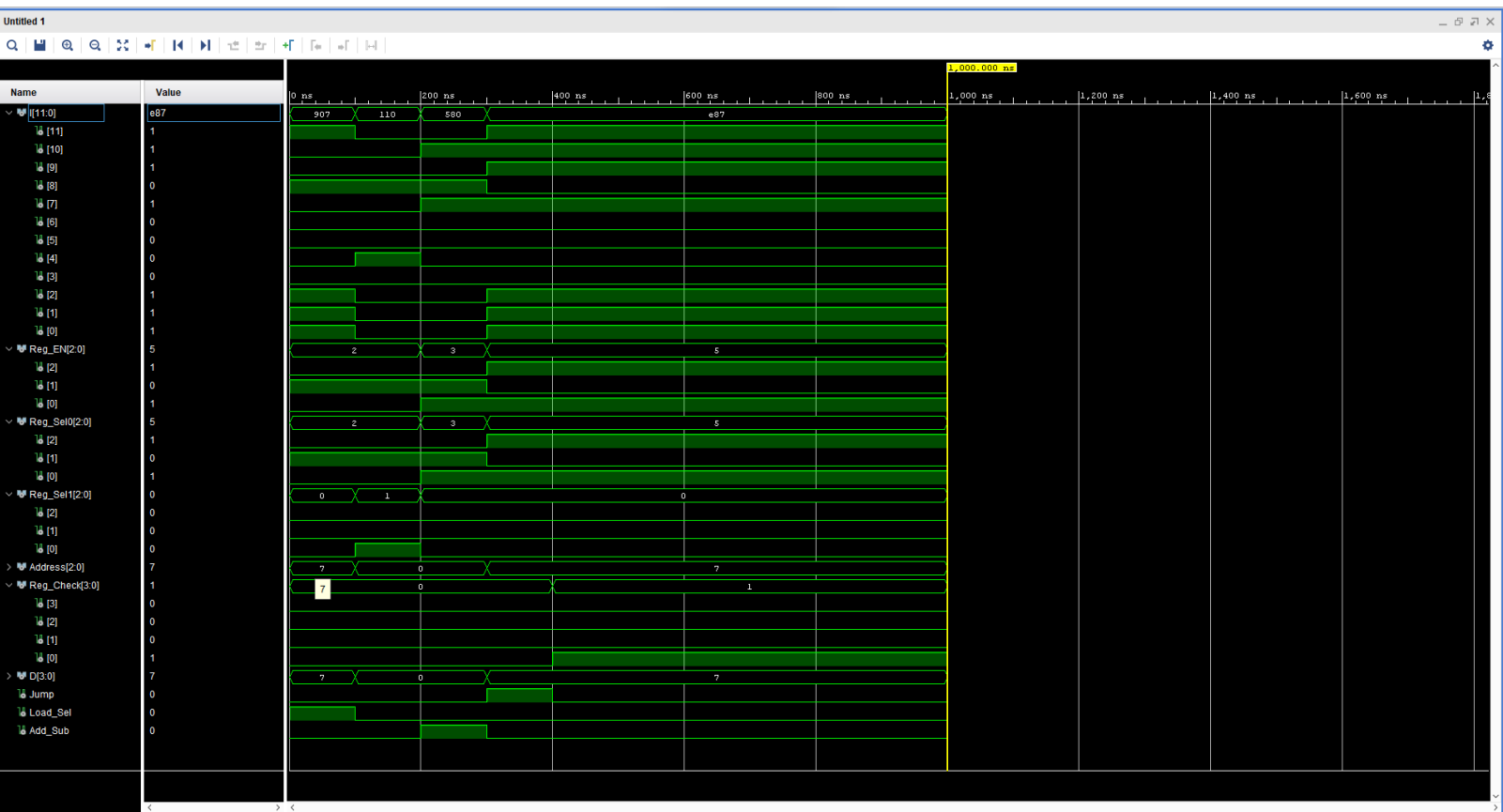

- **Reg Bank.**

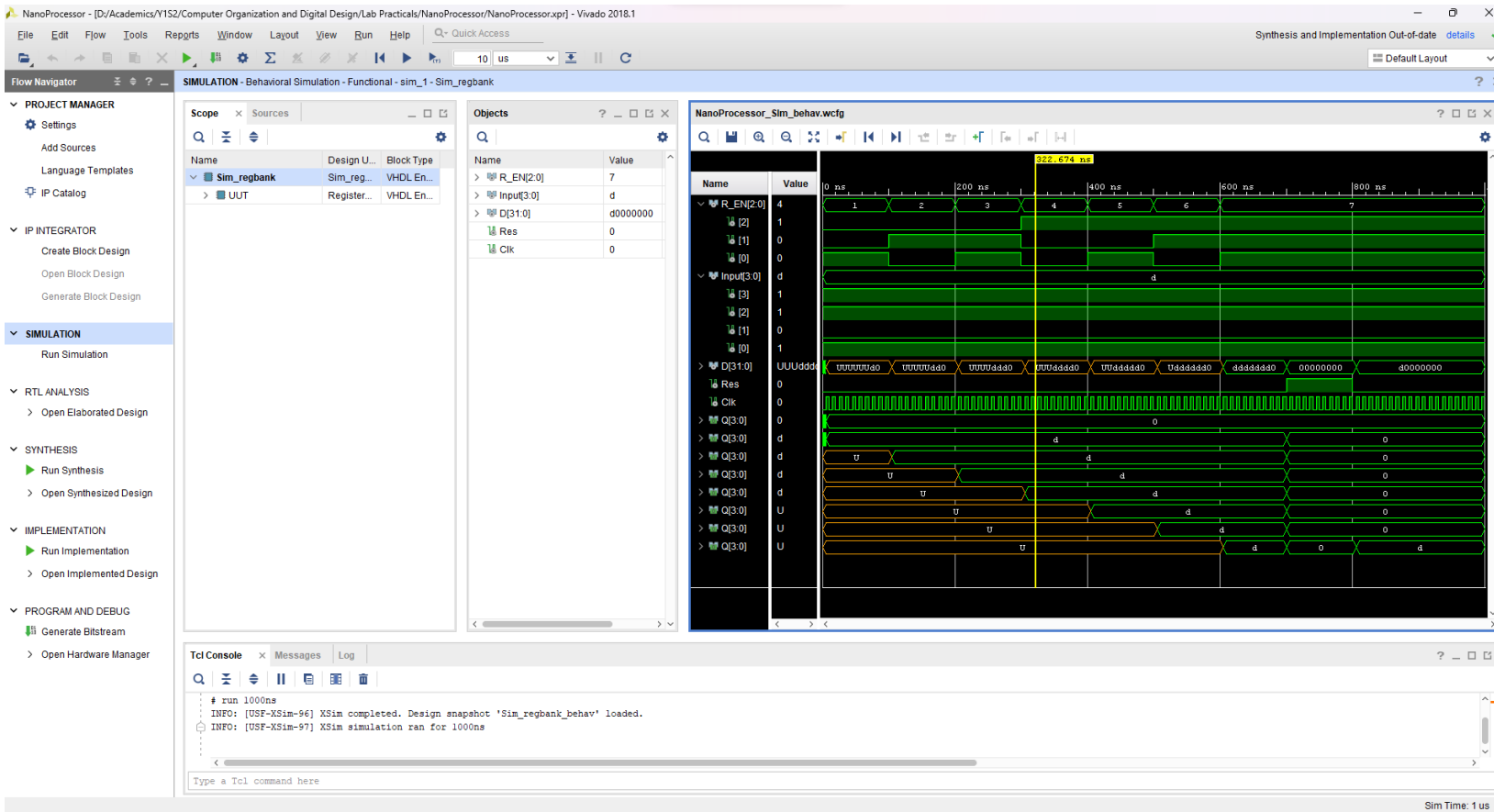

- **Program Counter.**

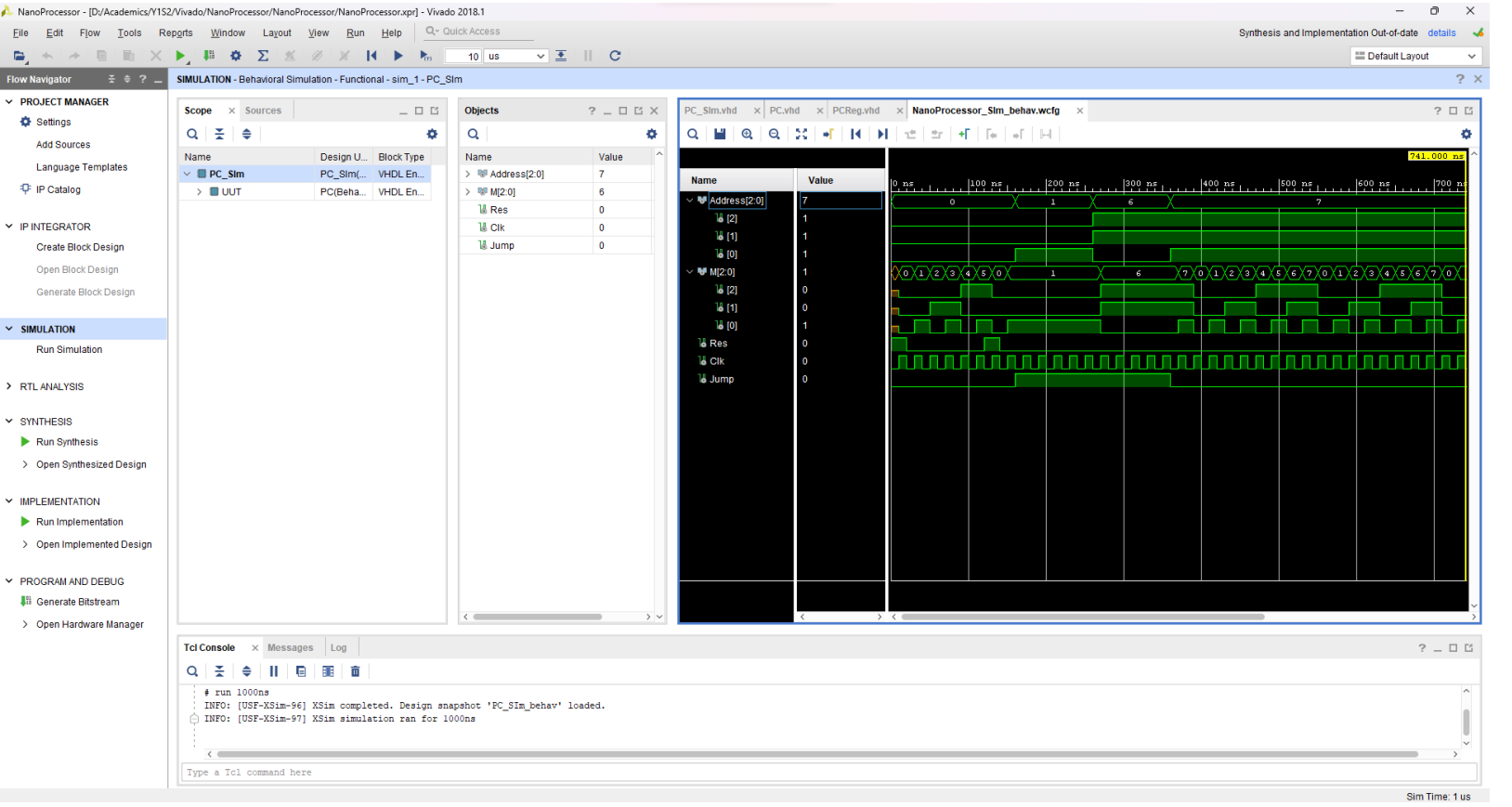

Conclusion.

We were able to practice team-working skills and improve communication, coordination, sharing responsibilities and integrating components developed by different team members. We were able to design our very own 4-bit arithmetic unit that can add and subtract signed integers, decode instructions to activate different components of the processor and to verify the functionality of the nano-processor.

Contribution.

S.A.C.H.Gunapala 210190R	G.V.H.H.B.Jayarathna 210242F
Designed the Register Bank	Designed the 4-bit Add/Sub unit
Designed all the Multiplexers inside the nano-processor	Designed 3-bit adder
Designed the Programmable ROM	Designed the Instruction Decoder
Designed part of Program Counter	Designed part of Program Counter.
Simulated the related components	Simulated the related components

Designing each component and connecting them took about 12 hours. Creating Test Bench files and simulating each component separately took about 6 hours. Connecting each component and simulating the Nano-Processor took 2 hours. Fixing bugs and optimizing the components for less logic gates took about another 10 – 12 hours. Spent about 30 – 32 hours completing the Nano-Processor.

NanoProcessor simulation VHDL.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
```

```

--library UNISIM;

--use UNISIM.VComponents.all;

entity NanoProcessor_SIm is
-- Port ( );
end NanoProcessor_SIm;

architecture Behavioral of NanoProcessor_SIm is
component NanoProcessor
    Port ( Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          Seg7input : out std_logic_vector (3 downto 0);
          OverFlow : out STD_LOGIC;
          Zero : out STD_LOGIC;
          Seg7output : out STD_LOGIC_VECTOR (6 downto 0);
          Anode : out std_logic_vector (3 downto 0));
end component;

signal Clk, Reset, OverFlow, Zero : std_logic;
signal Seg7output : std_logic_vector (6 downto 0);
signal Seg7input, Anode : std_logic_vector (3 downto 0);

begin

UUT: NanoProcessor port map (
    Clk => Clk,
    Reset => Reset,
    Seg7input => Seg7input,
    OverFlow => OverFlow,
    Zero => Zero,

```

```
Seg7output => Seg7output,  
Anode => Anode);
```

```
Clk_process : process  
begin  
Clk <= '0';  
wait for 5 ns;  
Clk <= '1';  
wait for 5 ns;  
end process;
```

```
processor : process  
begin  
Reset <= '0';  
wait for 250 ns;  
Reset <= '1';  
wait for 30 ns;  
Reset <= '0';  
wait;  
end process;
```

```
end Behavioral;
```